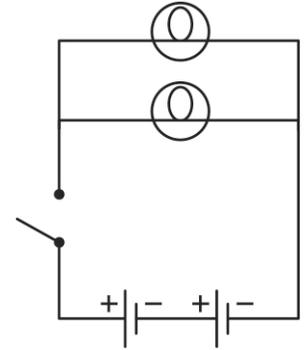


Part 2: Connecting bulbs in parallel

1. Create a circuit with two bulbs *in parallel*, as shown in the circuit diagram.
2. Compare the brightness of the bulbs in this circuit to the prior circuit with two bulbs in series.



Questions

- a. What property makes this a parallel circuit?
- b. How bright are the parallel bulbs compared to the series bulbs? Compared to the single bulb? Why?
- c. Unscrew one bulb from the parallel circuit. What happens to the brightness of the other bulb? Why?
- d. Is a series or parallel circuit better for connecting a string of lights? Why?
- e. Design a circuit of three bulbs that combines series and parallel arrangements, and sketch the circuit diagram. Predict the relative bulb brightness based on the previous experiments. Build the circuit and test your predictions. Were you correct?

Applying new knowledge

1. When resistors are connected in series:
 - a. Is their equivalent resistance smaller or larger than the individual resistances?
 - b. Is the current through them when connected together larger or smaller than their current if alone in the circuit?

2. When resistors are connected in parallel:
 - a. Is the combined resistance smaller or larger than the individual resistances?
 - b. Is the total current through the circuit larger or smaller than the total current if there were one resistor alone in the circuit?
 - c. Is the current through each individual resistor larger or smaller than the current if it was alone in the circuit?

3. Two strings of tree lights, each with a resistance of $200\ \Omega$, are connected together. What is their equivalent resistance if they are:
 - a. connected in series?
 - b. connected in parallel?

4. For two resistors with resistances of $10\ \Omega$ and $23.7\ \Omega$, what is the equivalent resistance if they are:
 - a. connected in series?
 - b. connected in parallel?

5. What would be the equivalent resistance if a third resistor of $12.8\ \Omega$ were:
 - a. added in series with them?
 - b. added in parallel with them?